


High Performance Computing Platform: #5 Design of High Performance Calculation Units

Renyuan ZHANG


Comp-Arch-Lab, Division of Info. Sci., NAIST

MOS Transistors

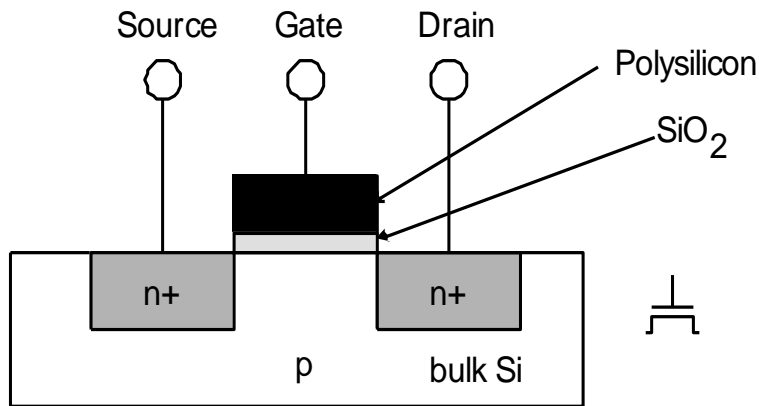- Four terminal device: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors (body is also called the substrate)
 - SiO_2 (oxide) is a “good” insulator (separates the gate from the body)
 - Called metal–oxide–semiconductor (MOS) capacitor, even though gate is mostly made of poly-crystalline silicon (polysilicon)




➤ **NMOS**

 

➤ **PMOS**


NMOS Operation

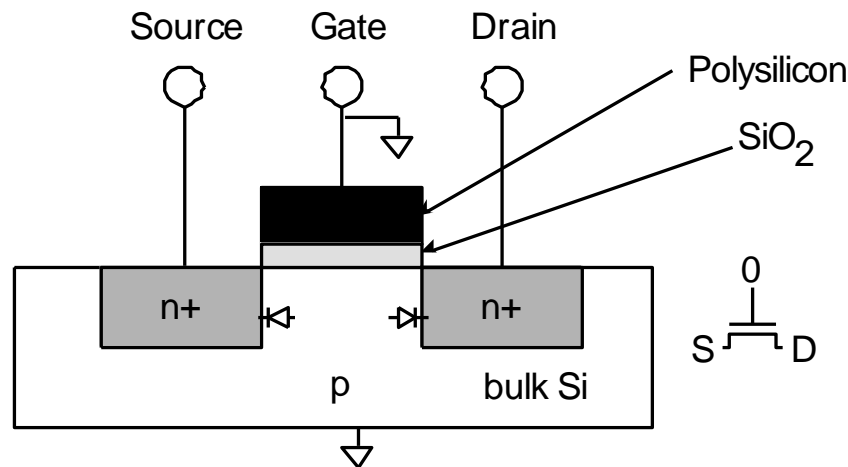- Body is commonly tied to ground (0 V)
- Drain is at a higher voltage than Source
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body “diodes” are OFF
 - No current flows, transistor is OFF




NMOS Operation Cont.

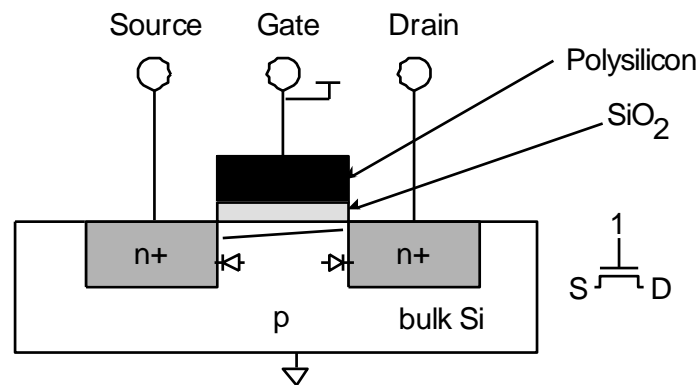- When the gate is at a high voltage: Positive charge on gate of MOS capacitor
 - Negative charge is attracted to body under the gate
 - Inverts a channel under gate to “n-type” (N-channel, hence called the NMOS) if the gate voltage is above a threshold voltage (V_T)
 - Now current can flow through “n-type” silicon from source through channel to drain, transistor is ON



PMOS Transistor

 - Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Drain is at a lower voltage than the Source
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- $GND = 0\text{ V}$
- In 1980's, $V_{DD} = 5\text{V}$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0,$
- Effective power supply voltage can be lower due to IR drop across the power grid.



Transistors as Switches

 - In Digital circuits, MOS transistors are electrically controlled switches
- Voltage at gate controls path from source to drain





CMOS Inverter

A	Y
0	
1	

  

CMOS Inverter



A	Y
0	
1	0

  

➤ Y is pulled low by the turned on NMOS Device. Hence NMOS is the pull-down device.

CMOS Inverter

A	Y
0	1
1	0

  

➤ Y is pulled high by the turned on PMOS Device. Hence PMOS is the pull-up device.

Power & energy

- Source of power dissipation

- $P = P_{\text{switching}} + P_{\text{short-circuit}} + P_{\text{leakage}} + P_{\text{static}}$

- Definitions:

- Switching power $P = CV^2f\alpha$

- Short circuit power $P = I_{\text{sc}}V$

- Leakage power $P = I_{\text{leakage}}V$

- Static power $P = I_{\text{static}}V$

- α : switching activity factor

- Low power design would look at the trade-offs of the above issues

Power & energy

- **Warning!** In everyday language, the term “power” is used incorrectly in place of “energy”
- Power is **not** energy
- Power is **not** something you can run out of
- Power can **not** be lost or used up
- It is **not** a thing, it is merely a rate
- It can **not** be put into a battery any more than velocity can be put in the gas tank of a car

Power & energy

- Power supply provides energy for charging and discharging wires and transistor gates. The energy supplied is stored & then dissipated as heat.

$$P = dw / dt$$

*Power: Rate of work being done w.r.t time
Rate of energy being used*

$$P = E / \Delta t$$

Unit: Watts = Joules/seconds

- If a differential amount of charge dq is given a differential increase in energy dw , the potential of the charge is increased by:
- By definition of current: $I = dq / dt$ $V = dw / dq$

$$dw / dt = \frac{dw}{dq} \times \frac{dq}{dt} = P = V \times I$$

A very practical formulation!


$$w = \int_{-\infty}^t P dt$$

Total energy

Power & energy

Switching Energy:
energy used to
switch a node

Calculate energy dissipated in
pullup:

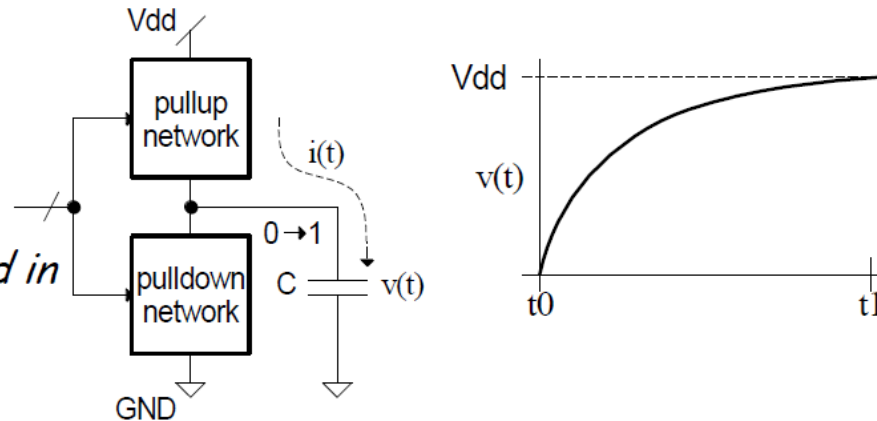


$$\begin{aligned}
 E_{sw} &= \int_{t_0}^{t_1} P(t) dt = \int_{t_0}^{t_1} (V_{dd} - v) \cdot i(t) dt = \int_{t_0}^{t_1} (V_{dd} - v) \cdot c (dv/dt) dt = \\
 &= cV_{dd} \int_{t_0}^{t_1} dv - c \int_{t_0}^{t_1} v \cdot dv = \underbrace{cV_{dd}^2}_{\text{Energy supplied}} - \underbrace{1/2cV_{dd}^2}_{\text{Energy stored}} = \boxed{1/2cV_{dd}^2} \quad \underbrace{\hspace{10em}}_{\text{Energy dissipated}}
 \end{aligned}$$

An equal amount of energy is dissipated on pulldown


Power & energy

- “Short Circuit” Current:

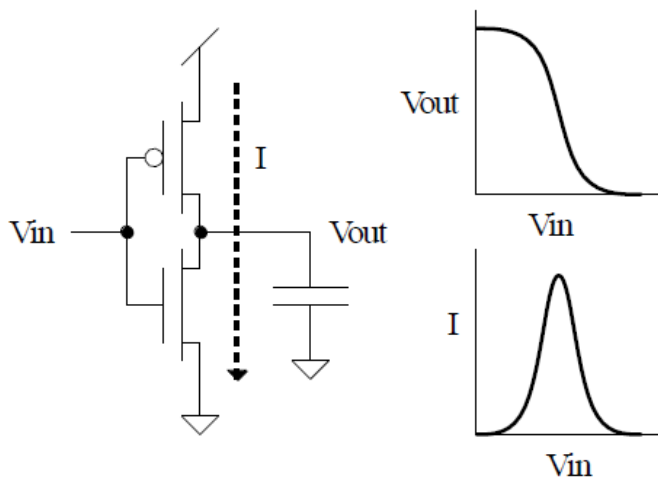


10-20% of total chip power

- ⌘ Junction Diode Leakage :

 

 Transistor drain regions
“leak” charge to substrate.



~1nWatt/gate
few mWatts/chip


DVS

Dynamic Voltage Scaling **must**
be along with V_{th} scaling!

DVS

Dynamic Voltage Scaling **must**
be made with trade-off between
ENERGY and speed!
NOT power v.s. Speed

DVS

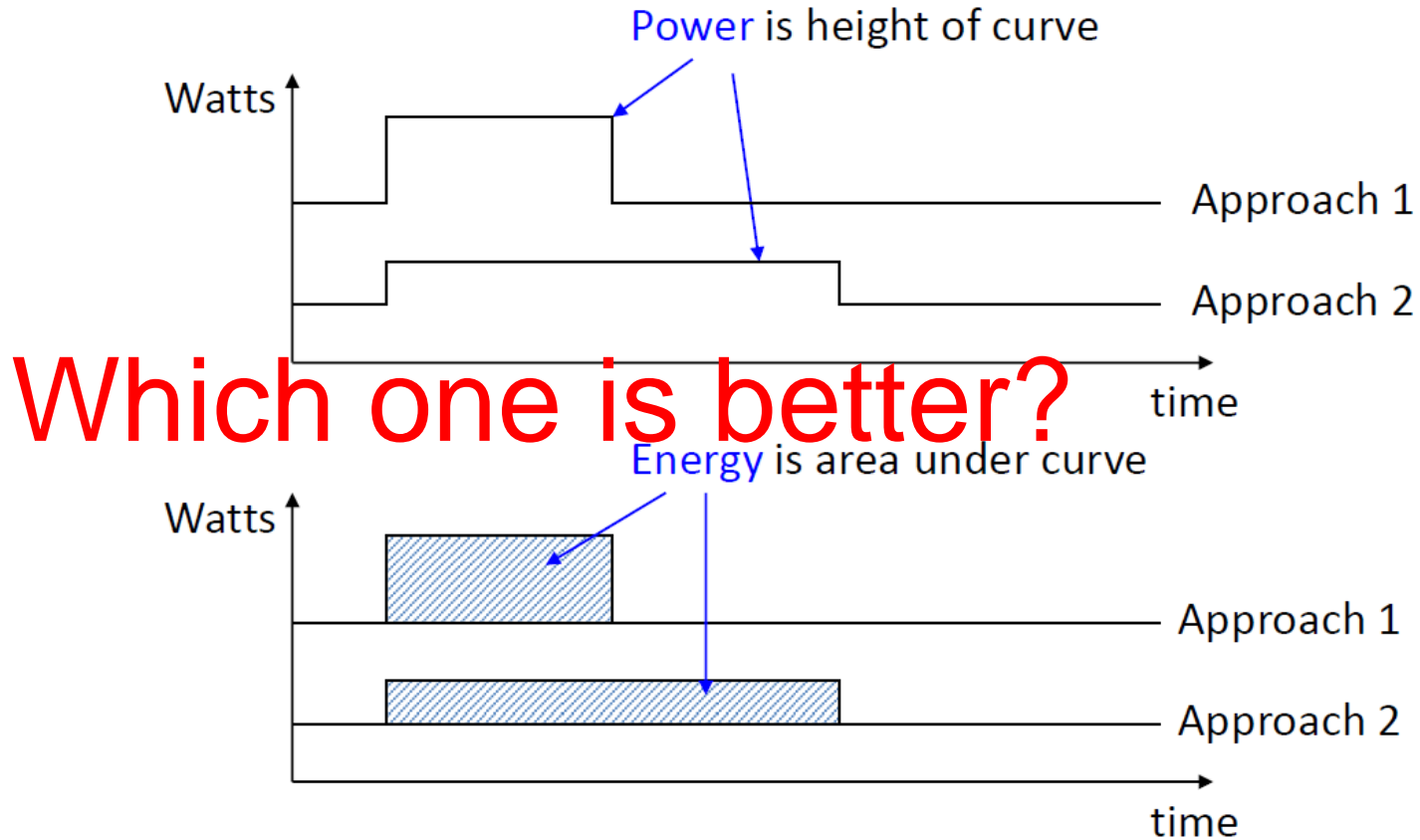

$$\text{Energy} = \text{Power} * \text{time for calculation} = \text{Power} * \text{Delay}$$

DVS

$$P = \alpha f C_L V_{DD}^2 + V_{DD} I_{peak} (P_{0 \rightarrow 1} + P_{1 \rightarrow 0}) + V_{DD} I_{leak}$$


Dynamic power
($\approx 40 - 70\%$ today
and decreasing
relatively)

Short-circuit power
($\approx 10\%$ today and
decreasing absolutely)

Leakage power
($\approx 20 - 50\%$ today
and increasing)


CMOS Gate Design

- A 4-input CMOS NOR gate

 

Complementary CMOS

 
- Complementary CMOS logic gates
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - a.k.a. static CMOS



	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

Series and Parallel

 - nMOS: 1 = ON
- pMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON




Conduction Complement

- Complementary CMOS gates always produce 0 or 1

- Ex: NAND gate

 - Series nMOS: $Y=0$ when both inputs are 1
- Thus $Y=1$ when either input is 0
- Requires parallel pMOS




- Rule of *Conduction Complements*

- Pull-up network is **complement** of pull-down
- Parallel \rightarrow series, series \rightarrow parallel

Compound Gates

- *Compound gates* can do any inverting function

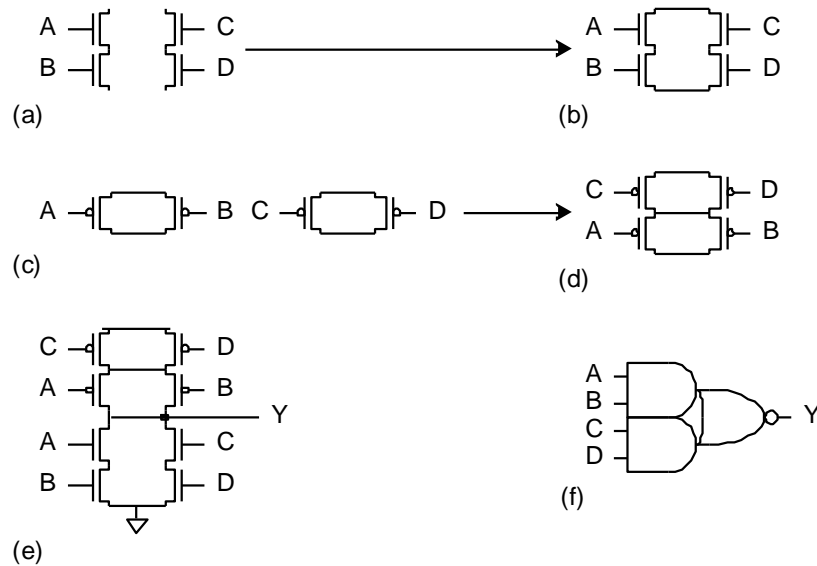- Ex: AND-AND-OR-INV (AOI22) $Y = \overline{(A \bullet B) + (C \bullet D)}$



Example: O3A1


•

$$Y = \overline{(A + B + C)} \bullet D$$

Example: O3AI



•

$$Y = \overline{(A + B + C)} \bullet D$$

 











Pass Transistors

- Transistors can be used as switches

  

Pass Transistors

- Transistors can be used as switches

          

Signal Strength


- *Strength* of signal
 - How close it approximates ideal voltage source
- V_{DD} and GND rails are strongest 1 and 0
- nMOS pass strong 0
 - But degraded or weak 1
- pMOS pass strong 1
 - But degraded or weak 0
- Thus NMOS are best for pull-down network
- Thus PMOS are best for pull-up network

Transmission Gates

- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well

Transmission Gates


 
- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well



Tristates


- *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  


Nonrestoring Tristate

 - Transmission gate acts as tristate buffer
 - Only two transistors
 - But *nonrestoring*
 - Noise on A is passed on to Y (after several stages, the noise may degrade the signal beyond recognition)




Tristate Inverter

 - Tristate inverter produces restored output
- Note however that the Tristate buffer
 - ignores the conduction complement rule because we want a Z output





Tristate Inverter

 - Tristate inverter produces restored output
- Note however that the Tristate buffer
 - ignores the conduction complement rule because we want a Z output





CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  

CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  


3-input NAND Gate


- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0

3-input NAND Gate

 - Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



Complex Gate

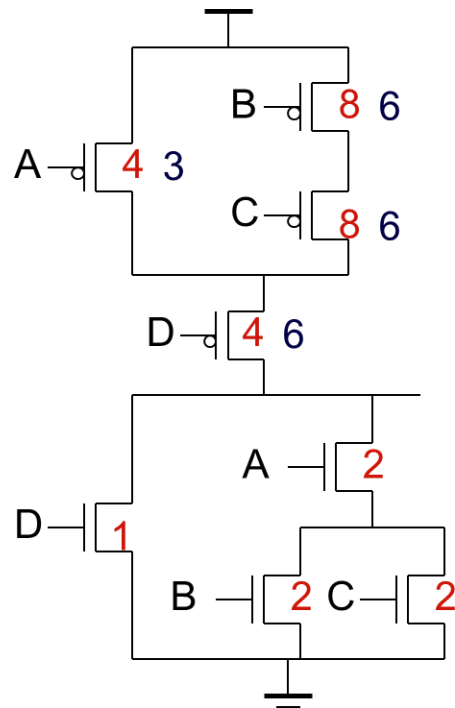


$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

Karnaugh maps


- The Karnaugh map is completed by entering a '1' (or '0') in each of the appropriate cells.
- Within the map, adjacent cells containing 1's (or 0's) are grouped together in twos, fours, or eights.

 Example

2-variable Karnaugh maps are trivial but can be used to introduce the methods you need to learn. The map for a 2-input OR gate looks like this:




A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

Example

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 

$$\bar{B} + A\bar{C}$$

HALF ADDER



Adding two bits

- We'll make a hardware adder based on our human addition algorithm.
- We start with a **half adder**, which adds two bits X and Y and produces a two-bit result: a **sum** S (the right bit) and a **carry out** C (the left bit).
- Here are truth tables, equations, circuit and block symbol.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C = XY$$

$$S = X'Y + XY'$$
$$= X \oplus Y$$

  

FULL ADDER

Adding three bits

- But what we really need to do is add *three* bits: the augend and addend bits, *and* the carry in from the right.
- A **full adder** circuit takes three inputs X , Y and C_{in} , and produces a two-bit output consisting of a sum S and a carry out C_{out} .
- This truth table should look familiar, as it was an example in the decoder and n

$$\begin{array}{rcccccc} & 1 & 1 & 1 & 0 & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ + & & & & & & \\ \hline & 1 & 1 & 0 & 0 & 1 & \end{array}$$

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full adder equations

- Using Boolean algebra, we can simplify S and C_{out} as shown here.

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 S &= \Sigma m(1,2,4,7) \\
 &= X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in} \\
 &= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in}) \\
 &= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' \\
 &= X \oplus Y \oplus C_{in}
 \end{aligned}$$



$$\begin{aligned}
 C_{out} &= \Sigma m(3,5,6,7) \\
 &= X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} \\
 &= (X'Y + XY')C_{in} + XY(C_{in}' + C_{in})
 \end{aligned}$$

- Notice that XOR operations simplify things a bit, but we had to resort to using algebra since it's hard to find XOR-based expressions with K-maps.

Full adder circuit

- We write the equations this way to highlight the hierarchical nature of adder circuits—you can build a full adder by combining two half adders!
  
$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = (X \oplus Y) C_{in} + XY$$




Full Adder Design I

- Brute force implementation from eqns


$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 


Full Adder Design II

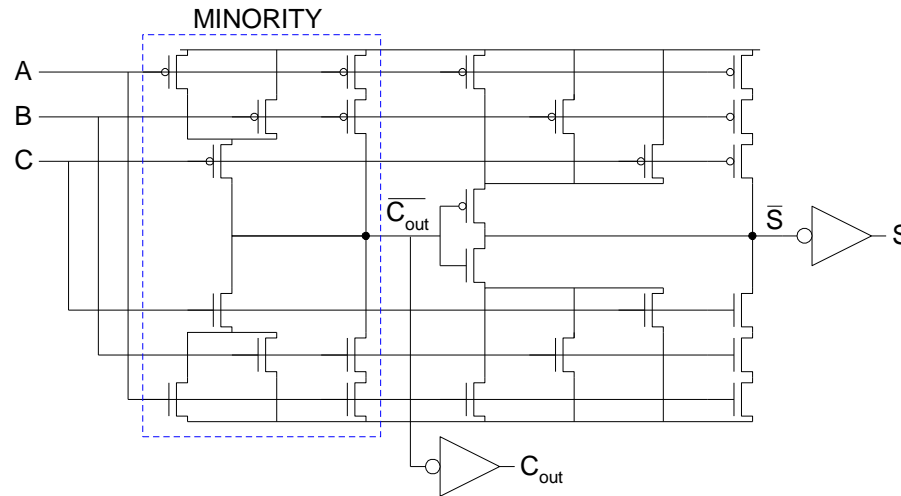- Factor S in terms of C_{out}
$$S = ABC + (A + B + C)(\sim C_{out})$$
- Critical path is usually C to C_{out} in ripple adder




Full Adder Design III

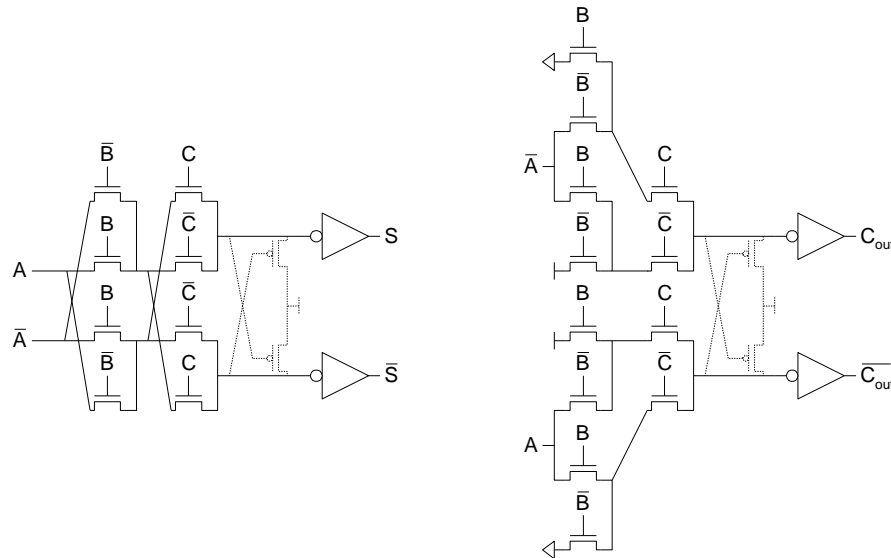
- Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area



A four-bit adder

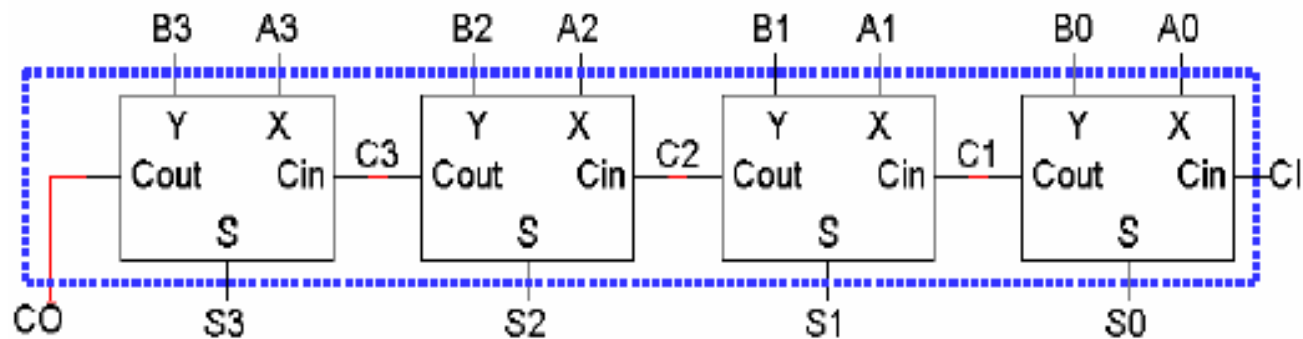


 - Similarly, we can cascade four full adders to build a four-bit adder.
 - The inputs are two four-bit numbers ($A_3A_2A_1A_0$ and $B_3B_2B_1B_0$) and a carry in C_1 .
 - The two outputs are a four-bit sum $S_3S_2S_1S_0$ and the carry out C_0 .
- If you designed this adder without taking advantage of the hierarchical structure, you'd end up with a 512-row truth table with five outputs!



An example of 4-bit addition

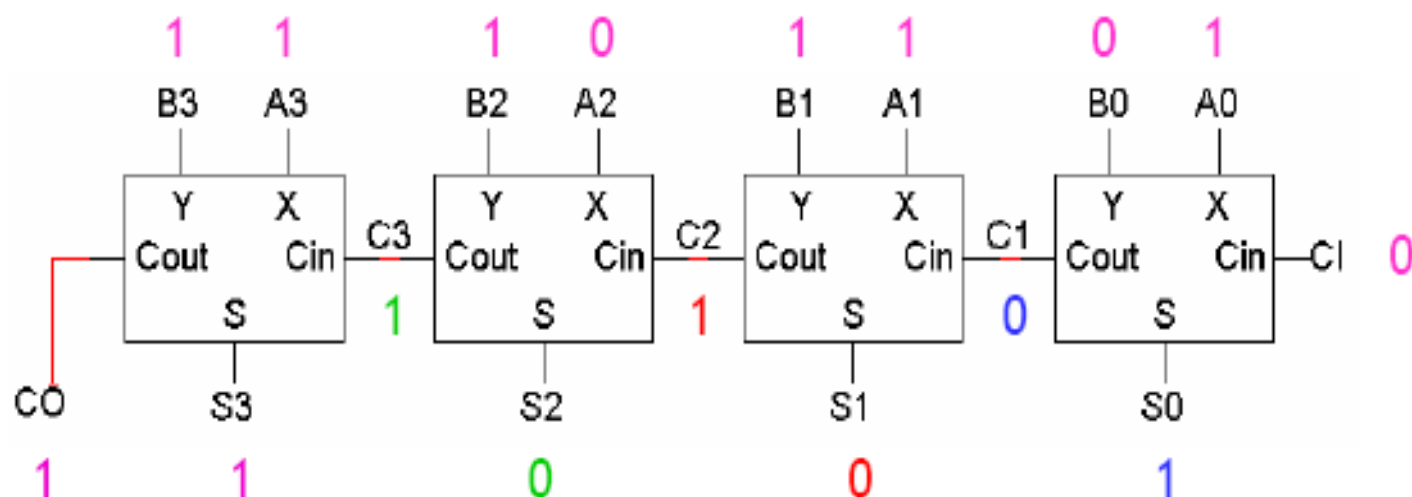
- Let's put our initial example into this circuit, with $A=1011$ and $B=1110$.



- Fill in all the inputs, including $C_i=0$
- The circuit produces C_1 and S_0 ($1 + 0 + 0 = 01$)
- Use C_1 to find C_2 and S_1 ($1 + 1 + 0 = 10$)
- Use C_2 to compute C_3 and S_2 ($0 + 1 + 1 = 10$)
- Use C_3 to compute C_0 and S_3 ($1 + 1 + 1 = 11$)

Ripple carry delays

- The diagram below shows our four-bit adder completely drawn out.
- This is called a **ripple carry adder**, because the inputs A_0 , B_0 and C_i “ripple” leftwards until C_0 and S_3 are produced.
- Ripple carry adders are slow!
 - There is a very long path from A_0 , B_0 and C_i to C_0 and S_3 .
 - For an n -bit ripple carry adder, the longest path has $2n+1$ gates.
 - The longest path in a 64-bit adder would include 129 gates!

 

PGK

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G =$
 - Propagate: $C_{out} = C$
 - $P =$
 - Kill: $C_{out} = 0$ independent of C
 - $K =$

PGK

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G = A \cdot B$
 - Propagate: $C_{out} = C$
 - $P = A \oplus B$
 - Kill: $C_{out} = 0$ independent of C
 - $K = \sim A \cdot \sim B$

A faster way to compute carry outs

- Instead of waiting for the carry out from each previous stage, we can minimize the delay by computing it directly with a two-level circuit.
- First we'll define two functions.
 - The "generate" function G_i produces 1 when there *must* be a carry out from position i (i.e., when A_i and B_i are both 1).


$$G_i = A_i B_i$$

- The "propagate" function P_i is true when an incoming carry is propagated (i.e, when $A_i=1$ or $B_i=1$, but not both).

$$P_i = A_i \oplus B_i$$

- Then we can rewrite the carry out function.

$$C_{i+1} = G_i + P_i C_i$$

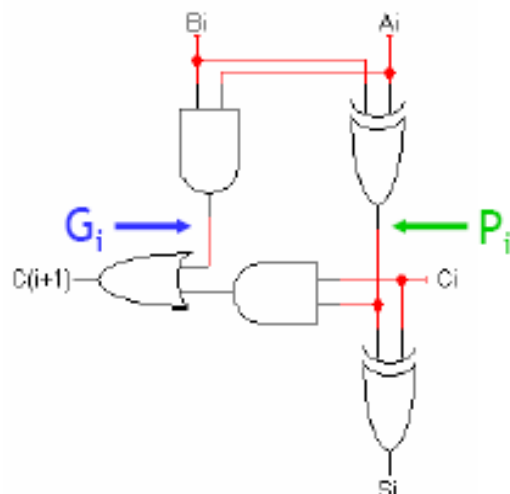

A_i	B_i	C_i	C_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

-
- Let's look at the carry out equations for specific bits, using the general equation from the previous page $C_{i+1} = G_i + P_i C_i$.


$$C_1 = G_0 + P_0 C_0$$


$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$


$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

 - These expressions are all sums of products, so we can use them to make a circuit with only a two-level delay.



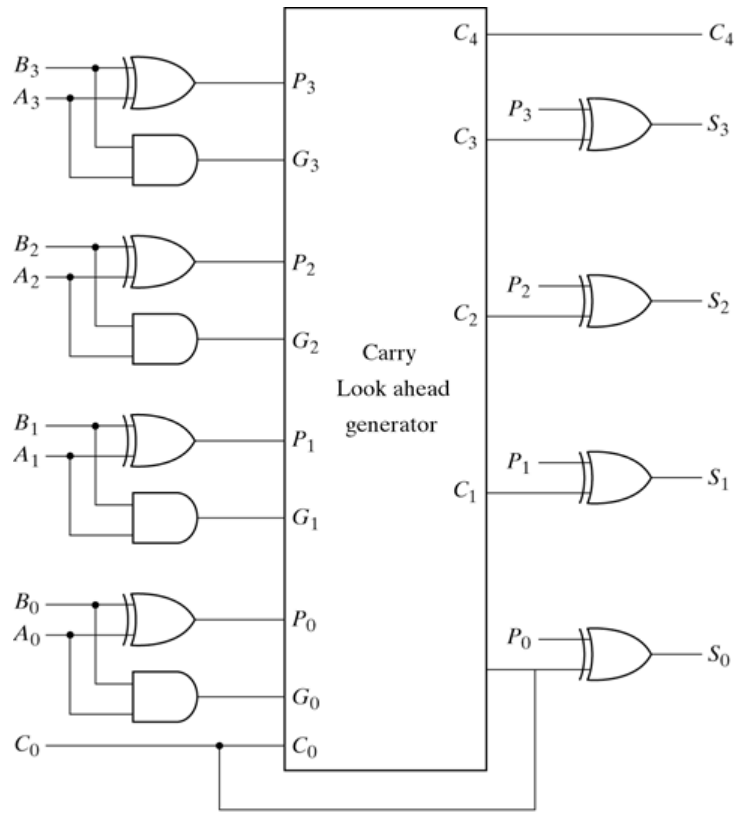


PG Logic

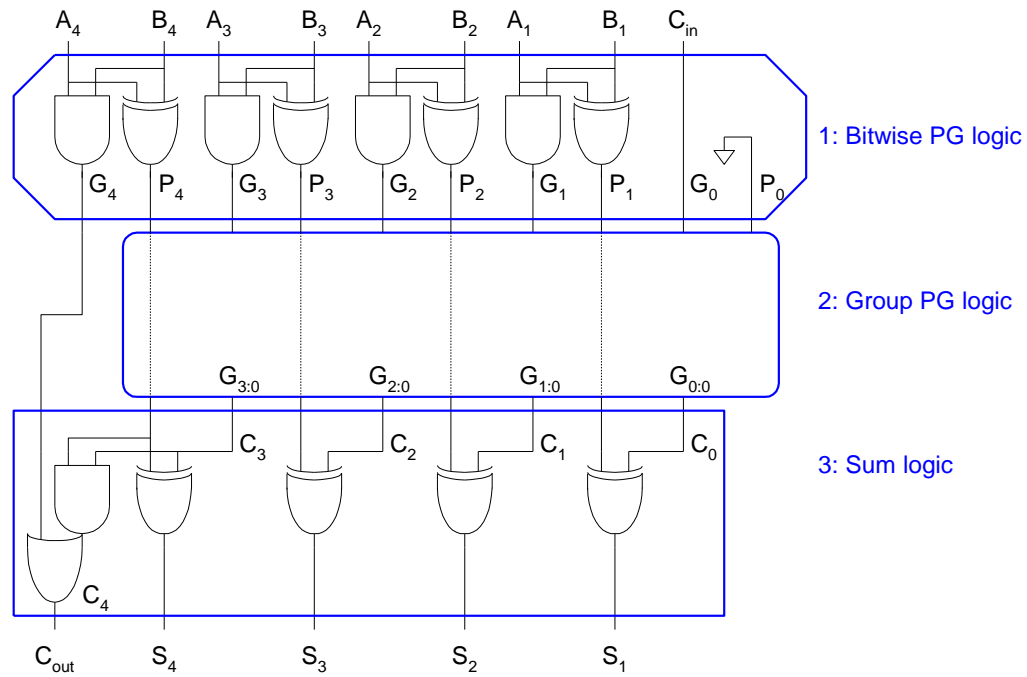


Carry-Ripple Revisited

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

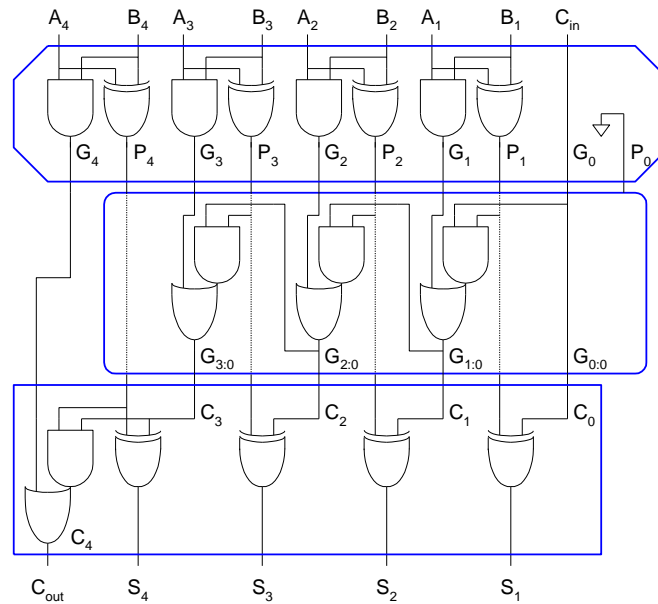


Carry-Ripple PG Diagram

$$t_{\text{ripple}} =$$

 


Carry-Ripple PG Diagram
 
$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{xor}$$




PG Diagram Notation





Black cell

 

Gray cell

 


Buffer

    


Carry-Skip Adder

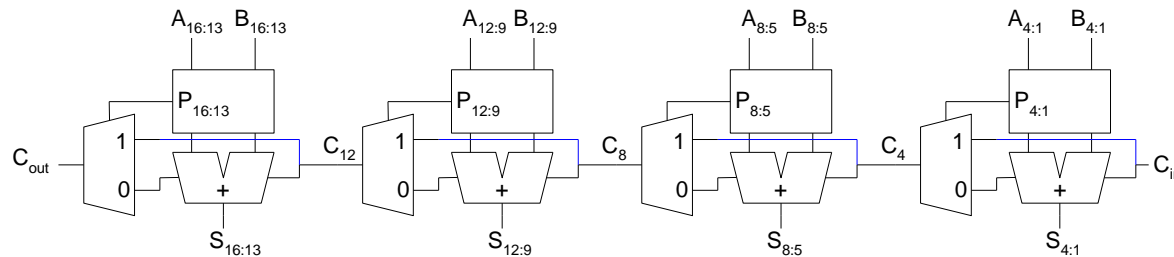- Carry-ripple is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal




Carry-Skip PG Diagram

 

For k n -bit groups ($N = nk$)

$$t_{\text{skip}} =$$

Carry-Skip PG Diagram

 


For k n -bit groups ($N = nk$)


$$t_{\text{skip}} = t_{pg} + [2(n-1) + (k-1)]t_{AO} + t_{\text{xor}}$$

Carry-Lookahead Adder

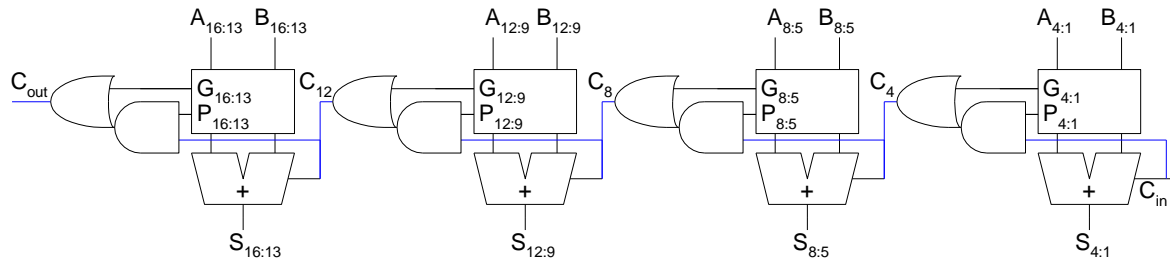
- Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- Uses higher-valency cells with more than two inputs.




CLA PG Diagram

 


Higher-Valency Cells

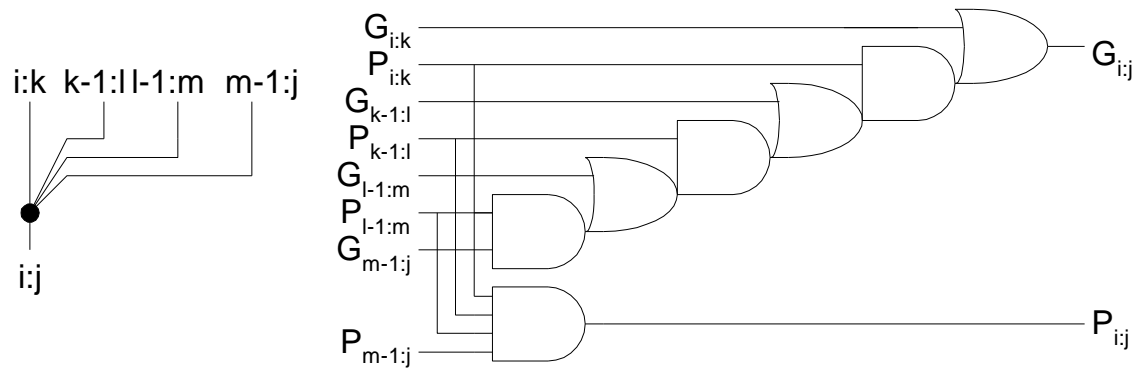


Brent-Kung

 

Sklansky

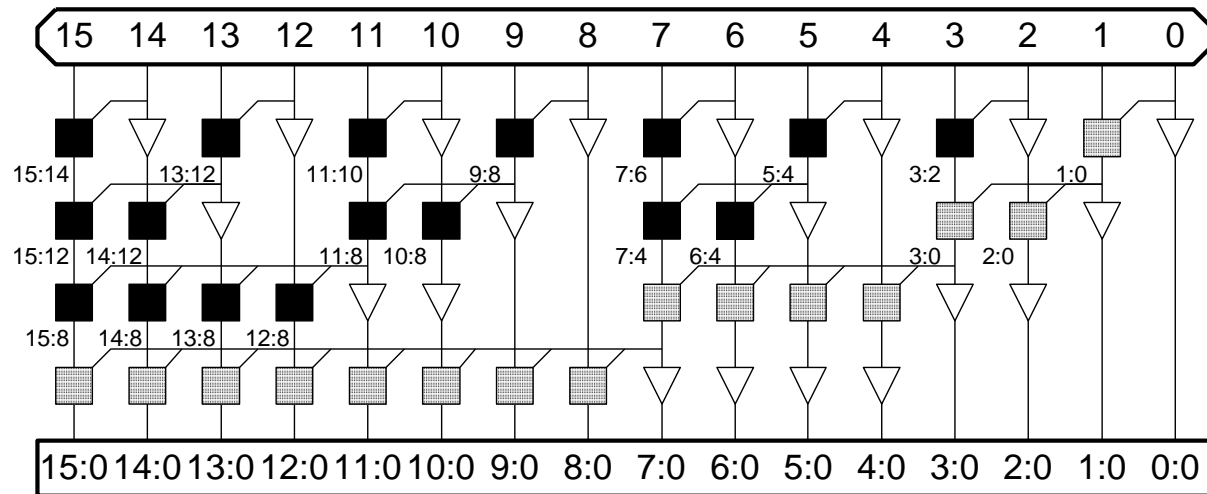

Kogge-Stone

 

Summary

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application.

Architecture	Logic Levels	Max Fanout	Cells
Carry-Ripple	$N-1$	1	N
Carry-Skip $n=4$	$N/4 + 5$	2	$1.25N$
Carry-Inc. $n=4$	$N/4 + 2$	4	$2N$
Brent-Kung	$2\log_2 N - 1$	2	$2N$
Sklansky	$\log_2 N$	$N/2 + 1$	$0.5 N \log_2 N$
Kogge-Stone	$\log_2 N$	2	$N \log_2 N$

End



Thank you very much.